


SUBJECT: Principle of Communications(PCE)

TOPIC: Pulse Amplitude Modulation(PAM)

CLASS: SE EXTC-A

MEMBERS:

SR.NO	NAME	ROLL.NO
1	Prajakta Lonkar	16104A0068
2	Savita Sonwane	16104A0071
3	Saili Panchal	16104A0066

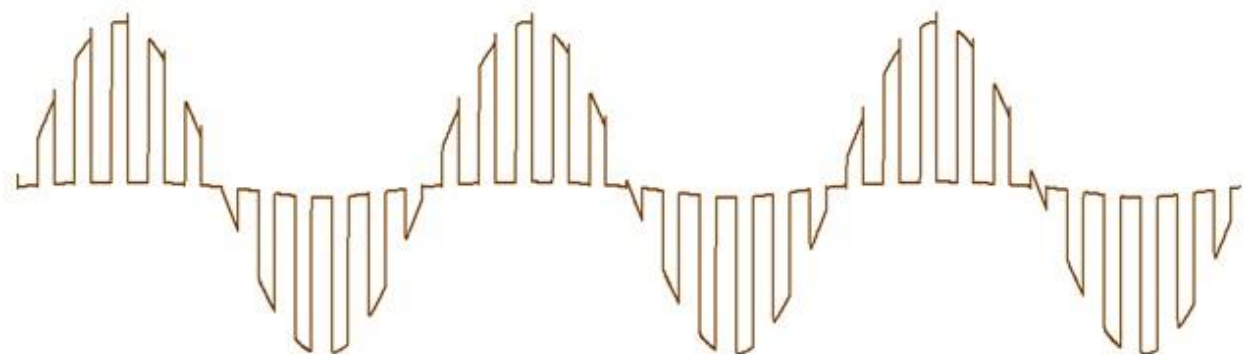

INTRODUCTION

- In PAM system, the amplitude of the pulsed carrier is changed in proportion with the instantaneous amplitude of the modulating signal $x(t)$. So the information is contained in the amplitude variation of PAM signal.
- The carrier is in the form of train of narrow pulses as shown below-


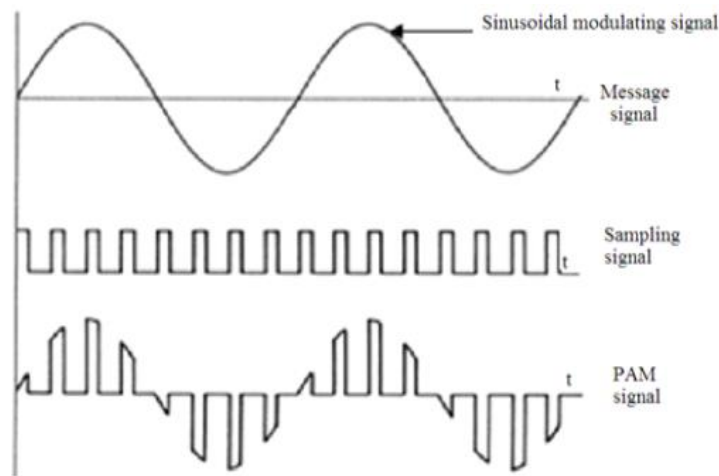


Fig2. Spectrum of PAM signal

- If we compare the process of PAM system with the sampling process, we will find that these two processes are identical.
- The PAM signal is sent by either wire or cable or it is used to modulate a carrier.

CIRCUIT DIAGRAM

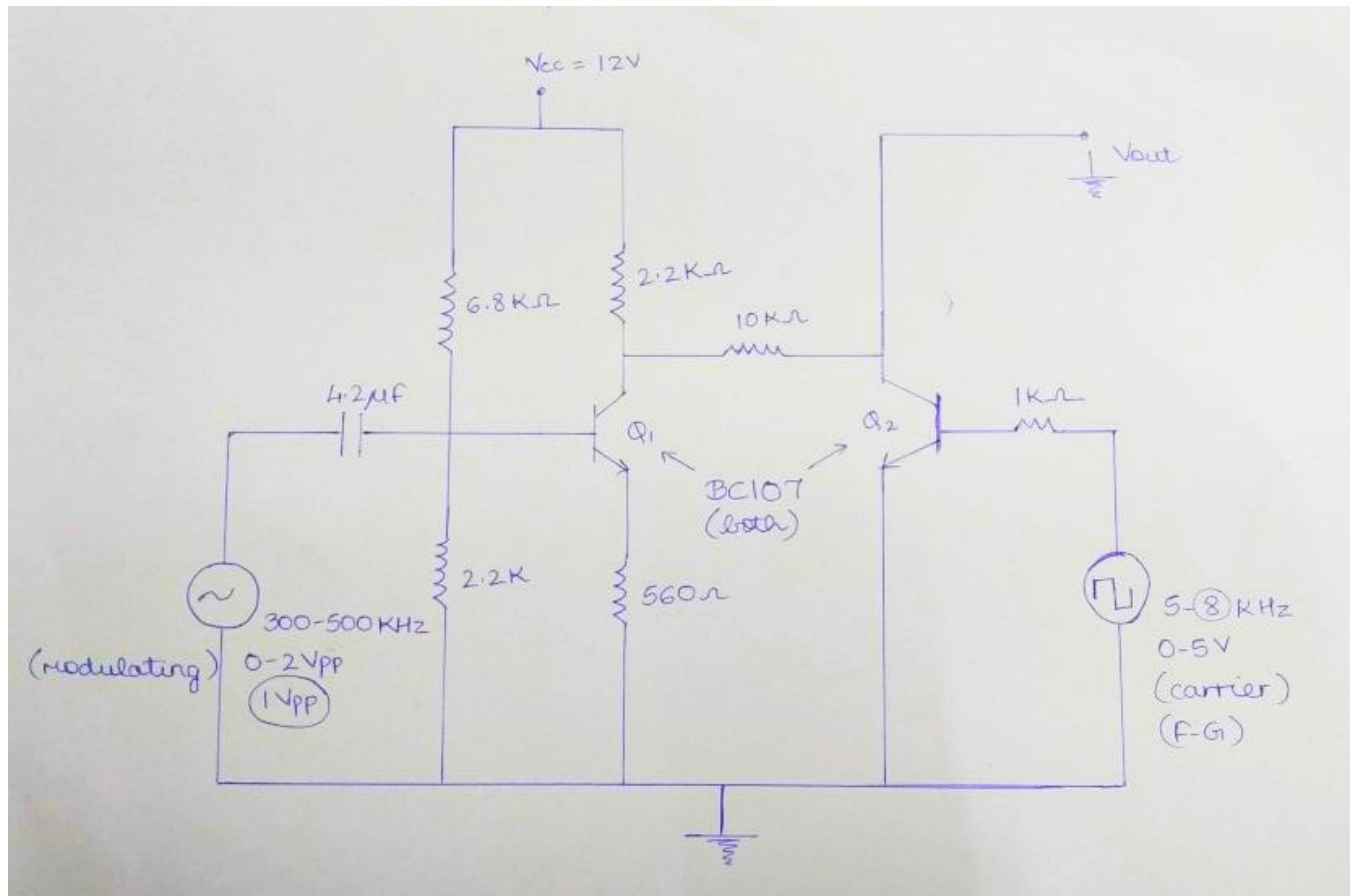

CIRCUIT EXPLANATION

The circuit consists of two Bipolar Junction Transistors (BJT) having voltage divider bias. The values of R_1 and R_2 of transistor Q1 are $6.8k\Omega$ and $2.2k\Omega$ respectively. Also the collector resistance R_c and emitter resistance R_e have values $2.2k\Omega$ and 560Ω respectively. The coupling capacitor C_{c1} has a value $4.2\mu F$.

The transistor Q2 has a resistor of $1k\Omega$ connected to its base. A resistor of $10k\Omega$ is connected between the collectors of Q1 and Q2.

The circuit is given a **Vcc** supply of **12V** and output is taken from the collector of Q2.

A **modulating signal** of **300-500kHz(0-2Vp-p)** is given at the base of Q1. **Carrier signal** of **5-8kHz(0-5V)** is given at the base of Q2.

STEPS:

- 1)** Initially connect $1k\Omega$ directly to ground and check whether sinusoidal signal is obtained at output.
- 2)** Give carrier signal.
- 3)** Take output across Q2(it will be inverted).

ADVANTAGES AND DISADVANTAGES

Applications of PAM:

- It is used in [Ethernet communication](#).
- It is used in many micro-controllers for generating the control signals.
- It is used in Photo-biology.
- It is used as an electronic driver for LED lighting.

Advantages:

- It is the simple process for both modulation and demodulation.
- Transmitter and receiver circuits are simple and easy to construct.
- PAM can generate other pulse modulation signals and can carry the message at the same time.

Disadvantages:

- Bandwidth should be large for transmission PAM modulation.
- Noise will be great.
- Pulse amplitude signal varies so power required for transmission will be more.

PRACTICAL OUTPUT

